

Department of Electrical & Computer Engineering


ECED – 3901 Design Methods II

Assignment #4

Due: July 6th, 2015 @ 12:30 PM - Submitted via BBLearn Website (PDF files only), OR printed files in 3901 Mail-Slot at ECED Office

1. Design a low-pass RC filter. The cut-off frequency of the filter in Hz is the lower four digits of your banner (B00) number. For example if your student ID is B00123456, you must design a low-pass filter with a cut-off frequency of 3456 Hz.
 - a) Specify the *ideal* resistor and capacitor values to achieve this cut-off frequency. Be sure to specify your cut-off frequency too!
 - b) Specify *actual* resistor and capacitor values. Use one of the capacitors in your design kit, and assume you have access to standard “5% tolerance” resistors (known as the E24 series).
 - c) Calculate the cut-off frequency of your *actual* filter under two conditions:
 - a. Assuming the resistor and capacitor values are as specified (i.e. a 2200 ohm resistor is actually 2200 ohms).
 - b. Assuming the capacitor value is as specified, but the resistor values are at the lower end of their allowed tolerance range, assuming 5% tolerance. A 2200 ohm resistor for example could *actually* be a $2200 * (1 - 0.05) = 2200 * 0.95 = 2090$ ohm resistor and ‘within tolerance’.
 - d) Using a circuit simulator, simulate the frequency response of the circuit from 0-20000 Hz. See <https://www.youtube.com/watch?v=EeH3h7NU66o&hd=1> for an example of how to use the LTSpice IV Circuit simulator (which you can download at <http://www.linear.com/designtools/software/> for Windows and Mac).
2. You have a desired signal at 550 Hz of 500 mV amplitude, and an undesired signal at 2 kHz of 2.2V amplitude.
 - 1) What is the *signal to noise ratio (SNR)* in dB? The SNR is simply calculated as $V_{\text{signal}} / V_{\text{noise}}$, where the ‘noise’ is the undesired signal here. Be sure when you convert to dB to use the correct dB conversion (i.e. - power vs. voltage), and be careful of ensuring you have the correct sign (i.e. – ratios less than one should be a *negative* sign).
 - 2) Your system specification says the SNR should be +12 dB. What should the *voltage ratio* be for the signal to noise?

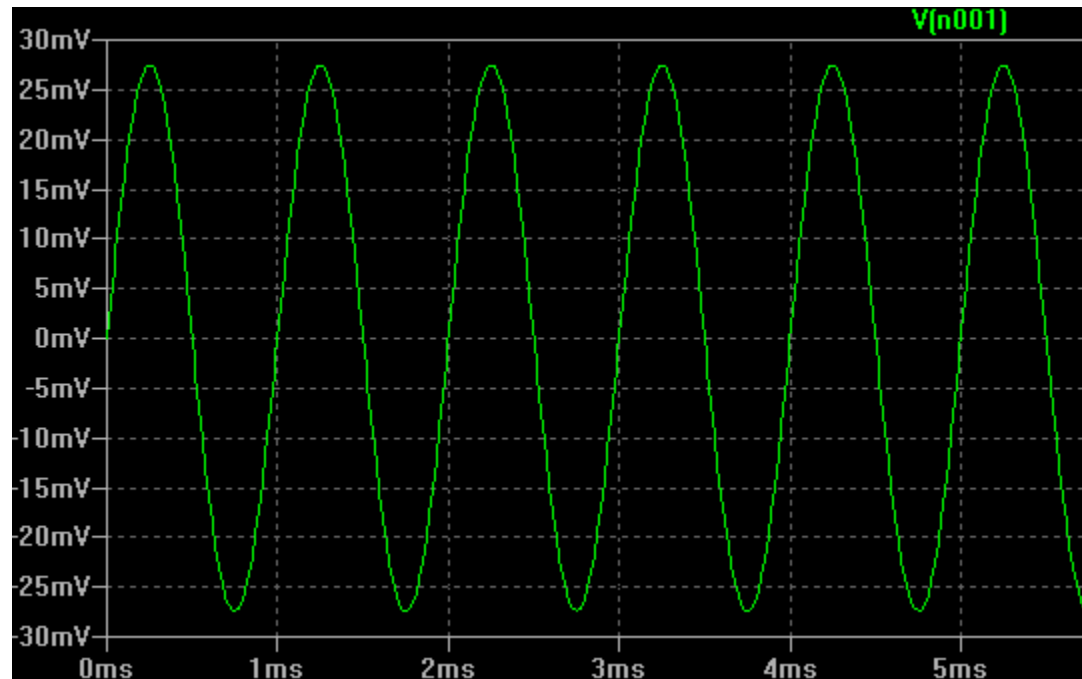- 3) Assuming your desired signal remains constant at 500mV, what is the amplitude reduction of the noise (2 kHz signal) in dB you require?
 - 4) Can you use a low-pass 1st order RC filter, to sufficiently suppress the undersigned signal to meet the design requirements? If so design such a filter. You must ensure the final **SNR** is at least 12dB, it's insufficient to *only* check the suppression of the noise at 2 kHz. Your filter may reduce the amplitude of the desired signal as well as the undesired signal, which does not actually improve the SNR, since the ratio between the signal/noise is not improving.
3. Design an op-amp circuit with the following characteristics:
- Power supply of the op-amp is single-ended, 10V supply.
 - Op-amp device is a TL-074
 - Input signal is a 0 - 55mV peak-to-peak, 1kHz, sine centered around 0-volts. The following shows a 55mV peak-to-peak signal – pay careful attention to peak-to-peak measurements, in this example the wave swings $\pm 27.5\text{mV}$.



- Desired output is a signal of around 2-5V indicating the amplitude of the sine wave, which will be fed into an AVR input. This means it must perform both amplification and envelope detection.
- Be sure to include the protection circuit to avoid blowing up the AVR input as required.
- Simulate the circuit for two conditions and include a graph of the output showing the output voltage:
 - No input (i.e. 0 mV peak-to-peak)
 - 40mV peak-to-peak.