

# ECED3901

# Design Methods II

---

LECTURE #4: DC MOTOR DRIVING

# What are we covering?

---


- DC Motors
  - Brushed
  - Brushless
- Driving Motors
  - Simple (On-Off)
    - Faraday's Law in real life
    - Snubbing / Diode Circuits
    - EMC Capacitor
  - Half-Bridge
  - Full-Bridge
- Transistors as Switches
  - Bipolar
  - MOSFET
- Driving transistors as switches

# DC Motor Types

---

# Motor Types: Brushed

---

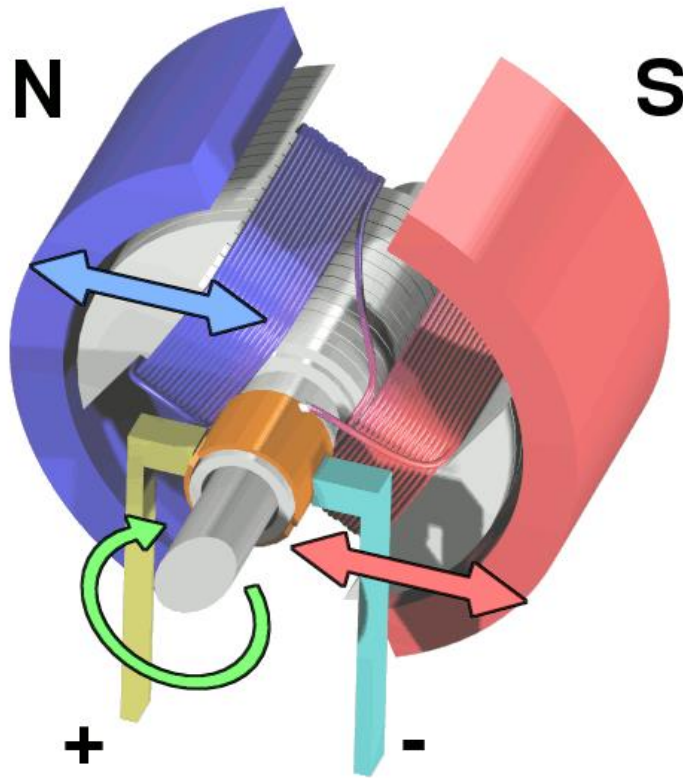

Source: [http://commons.wikimedia.org/wiki/File:Electric\\_motor\\_cycle\\_1.png](http://commons.wikimedia.org/wiki/File:Electric_motor_cycle_1.png)

# How DC Motors Work

---

**Note:** to avoid trying to draw complex diagrams, I'm instead going to refer you to this YouTube video for basics of the DC motor:

<https://www.youtube.com/watch?v=LAtPHANefQo>

If you view the video version of this lecture the video will be missing, but instead see the youtube video. Note we are only dealing with permanent motor stators (i.e. up to 2:50 in the video).

# Steady-State Operation

---

$$V_M = K_\omega \omega + I_a R. \quad (4.1)$$

In this equation,

$V_M$  = the applied motor voltage

$K_\omega$  = motor speed constant (volts per radians/sec)

$\omega$  = angular speed of the motor (radians/sec)

$I_a$  = armature current (this is the motor current)


$R$  = motor resistance (armature resistance + commutator resistance.

(4.2)

Source: Dr. Gregson's Design Methods II ECED 3901 Manual, 2005.


# Back-EMF Measurement

---

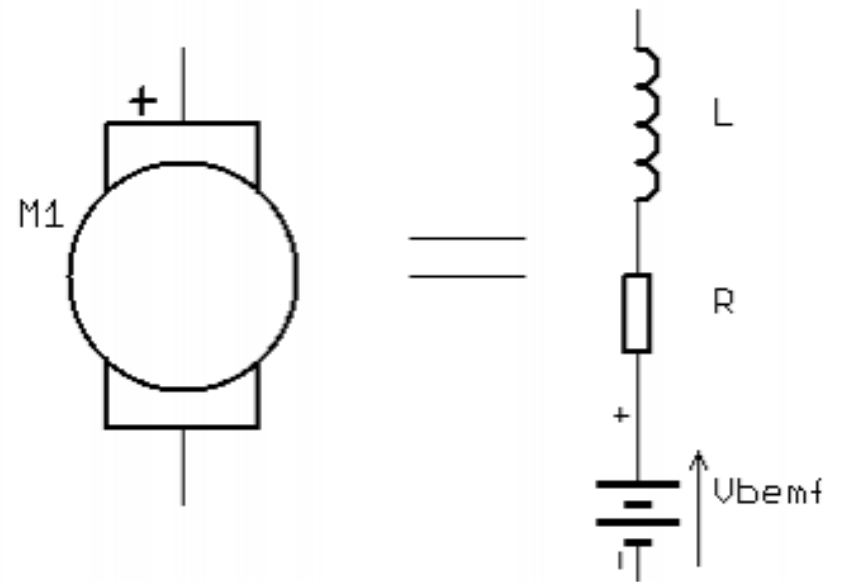

Source: <http://www.precisionmicrodrives.com/application-notes-technical-guides/application-bulletins/ab-021-measuring-rpm-from-back-emf>


# Back-EMF Measurement

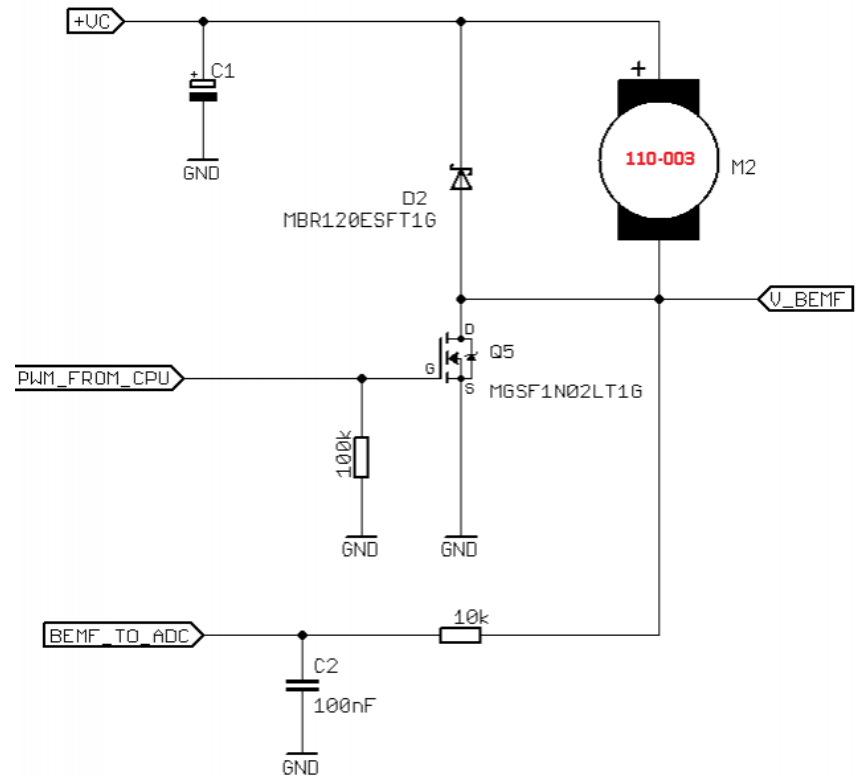

Source: <http://www.precisionmicrodrives.com/application-notes-technical-guides/application-bulletins/ab-021-measuring-rpm-from-back-emf>




# Back-EMF

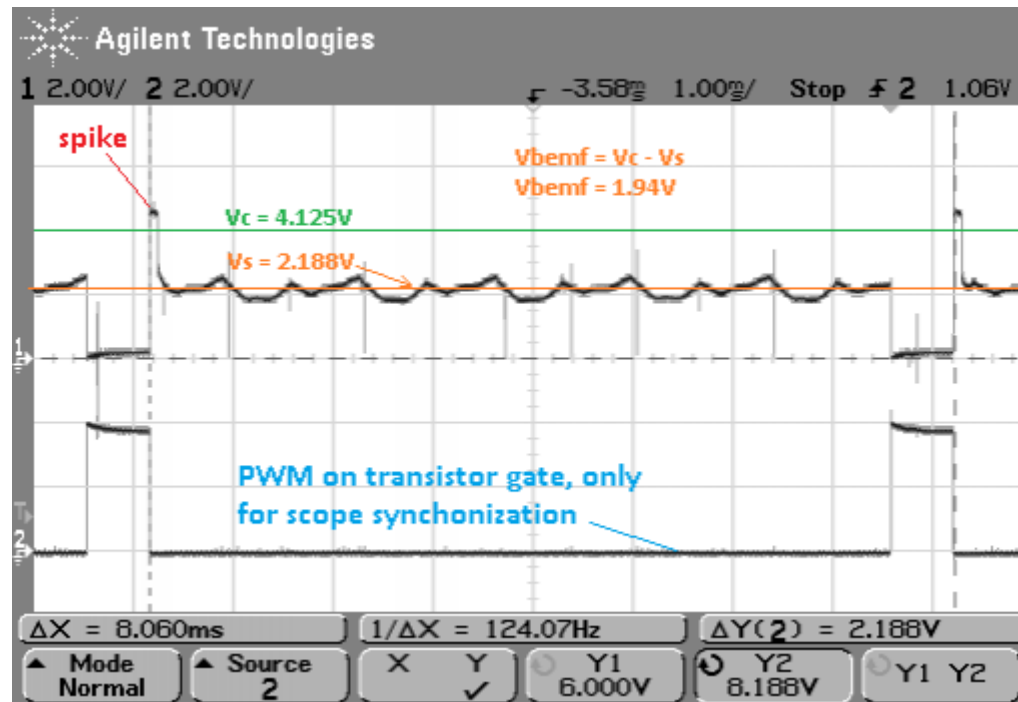

Source: <http://www.precisionmicrodrives.com/application-notes-technical-guides/application-bulletins/ab-021-measuring-rpm-from-back-emf>

# Back-EMF

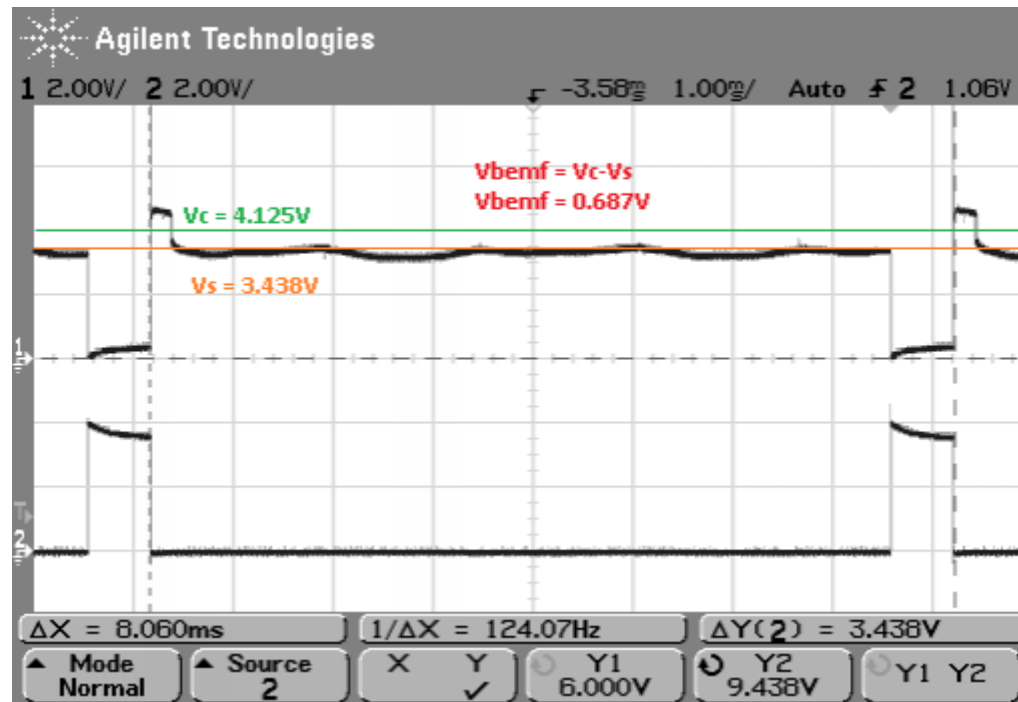

Source: <http://www.precisionmicrodrives.com/application-notes-technical-guides/application-bulletins/ab-021-measuring-rpm-from-back-emf>

# Motor Inductance

---

$$V = L \frac{di}{dt}$$

# Motor Inductance

---


# Additional Motor Dynamics

---

See Dr. Gregson's ECED3901 Manual for information on additional motor dynamics. Due to lecture timing this material is omitted from these lectures.

# Motor Types: Brushless

---

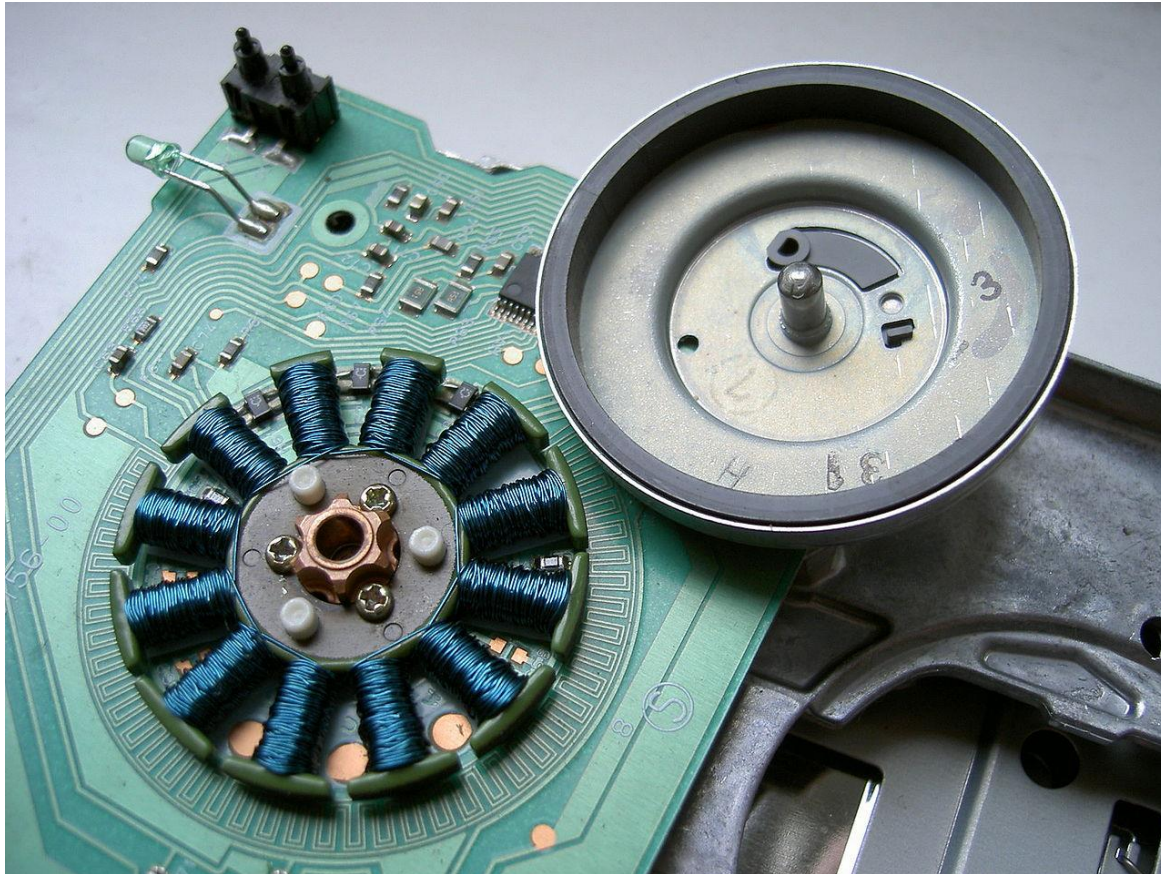


Source: [http://en.wikipedia.org/wiki/Brushless\\_DC\\_electric\\_motor#/media/File:Floppy\\_drive\\_spindle\\_motor\\_open.jpg](http://en.wikipedia.org/wiki/Brushless_DC_electric_motor#/media/File:Floppy_drive_spindle_motor_open.jpg)

# Driving DC Motors

---

# Driving a motor... easy!

---

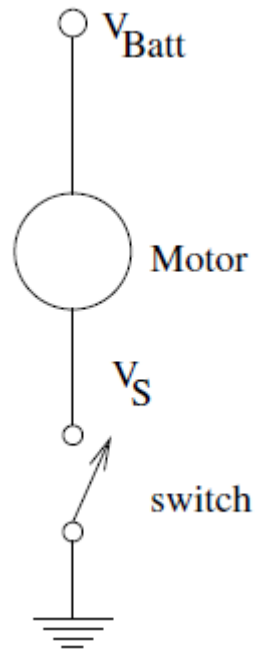


Source: Dr. Gregson's Design Methods II ECED 3901 Manual, 2005.



# Example Circuit


---



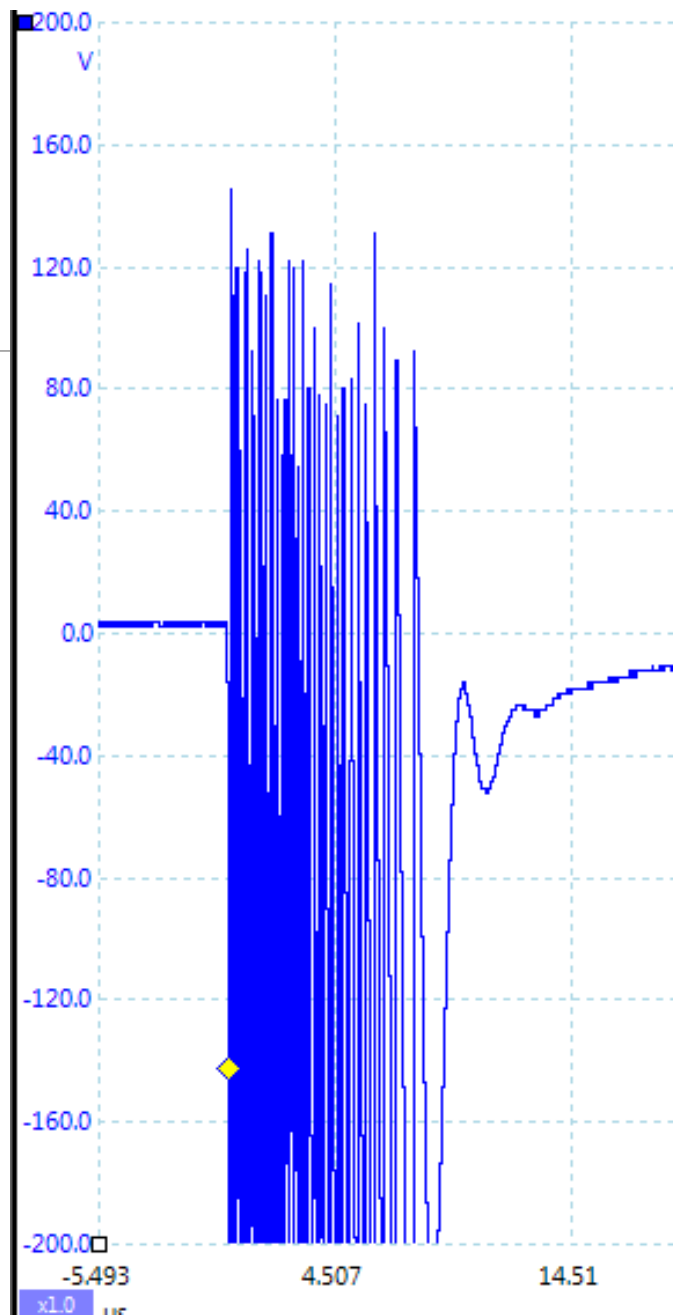


# Adding a Diode


---

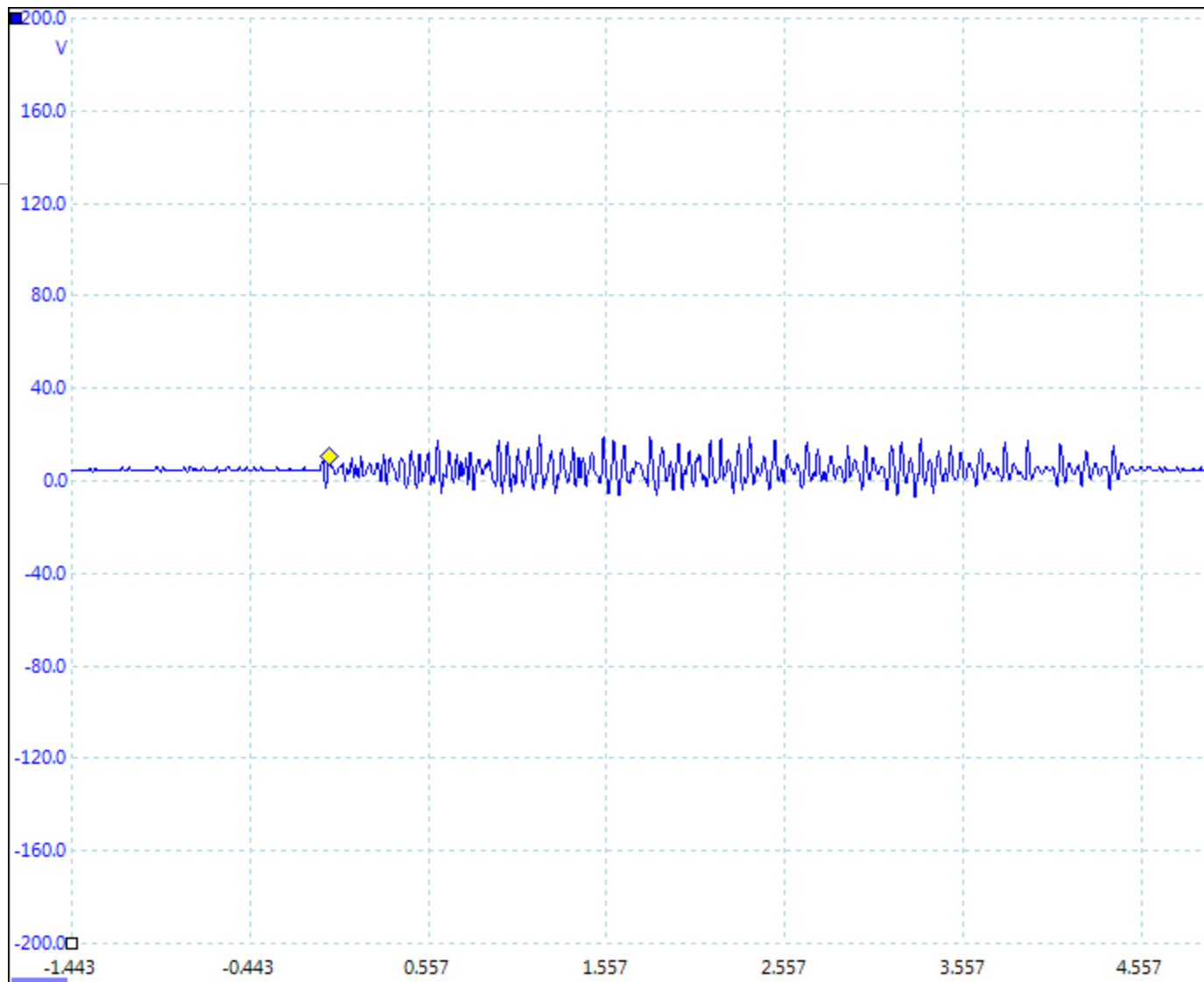

# Capacitor for Noise Suppression

---

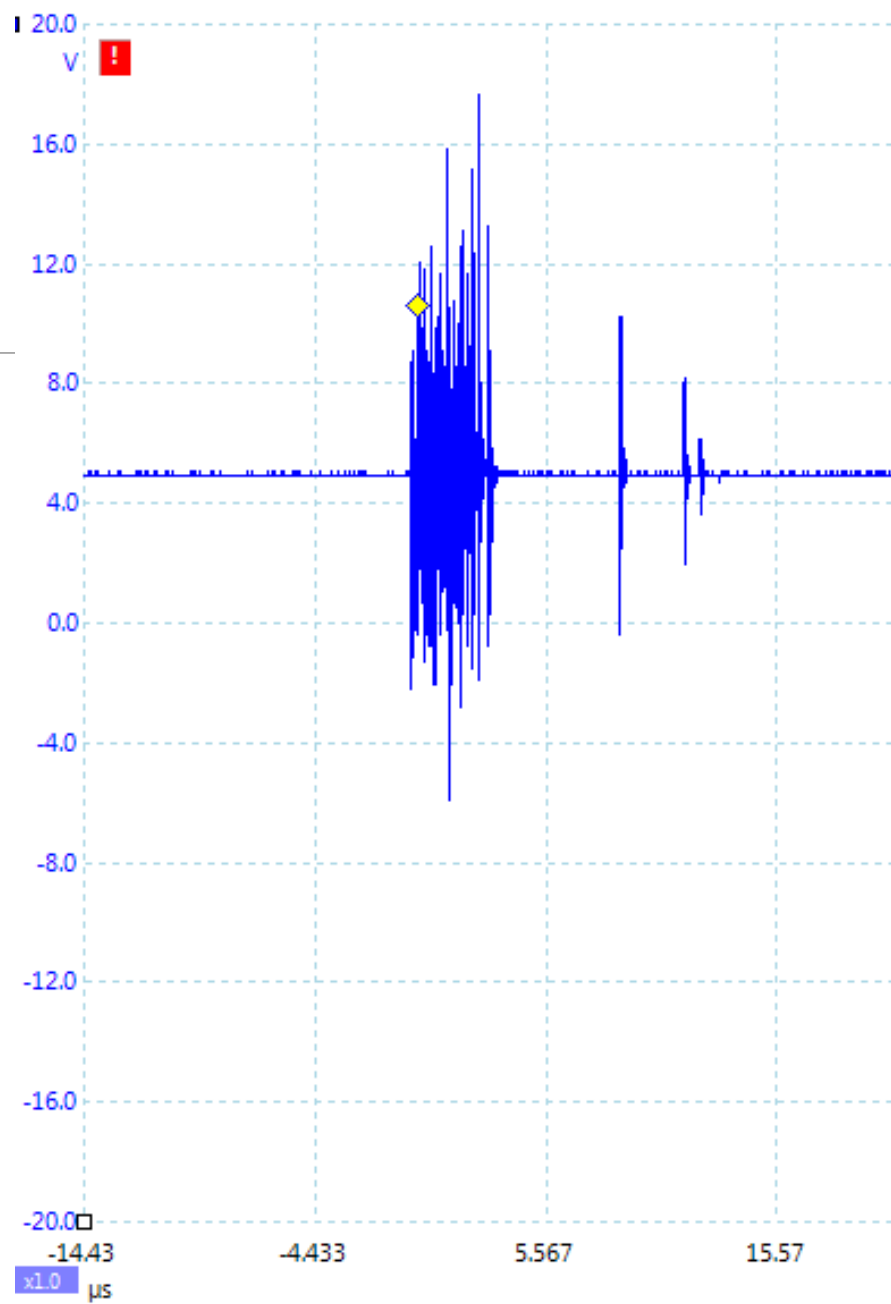


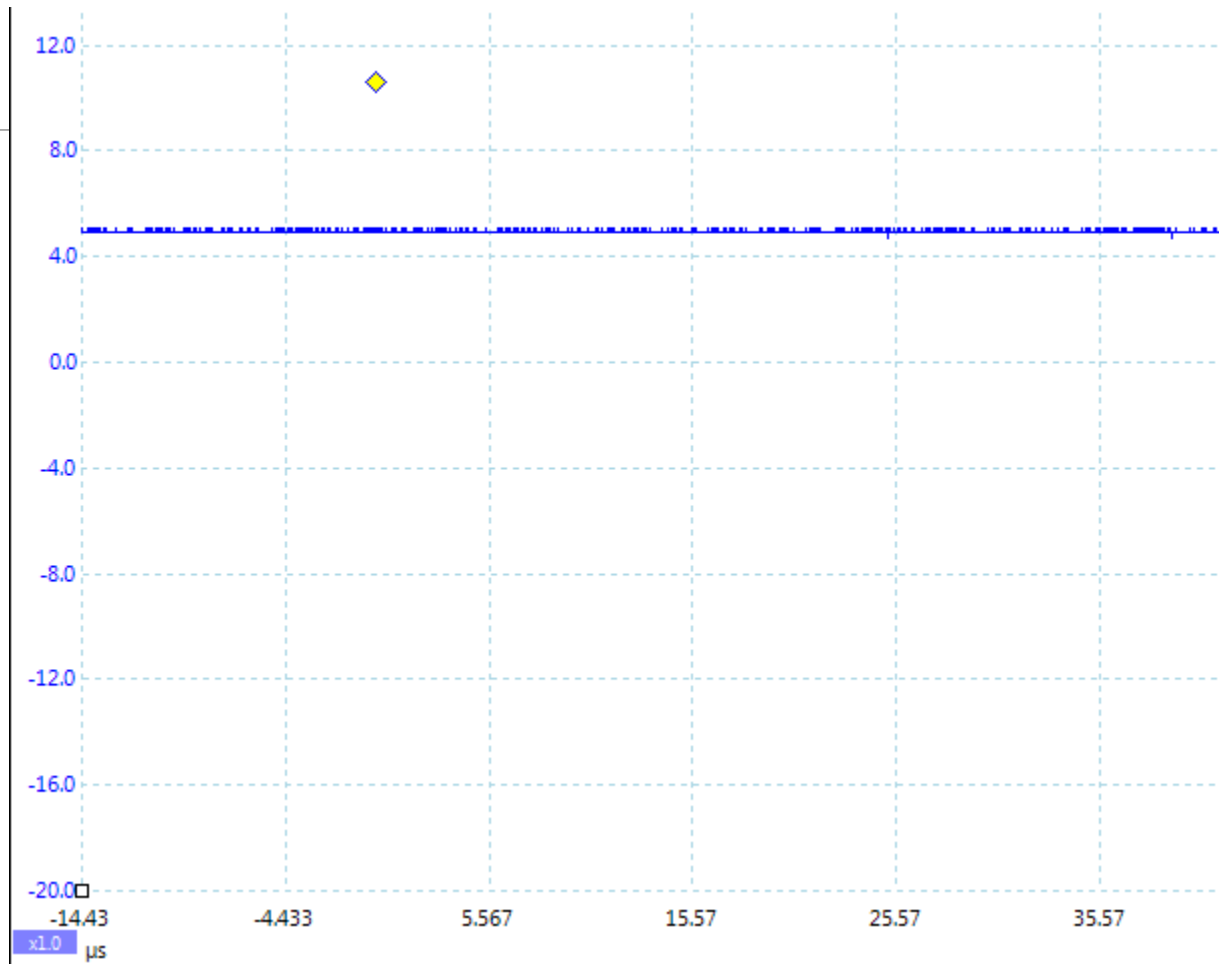




# Half-Bridge

---

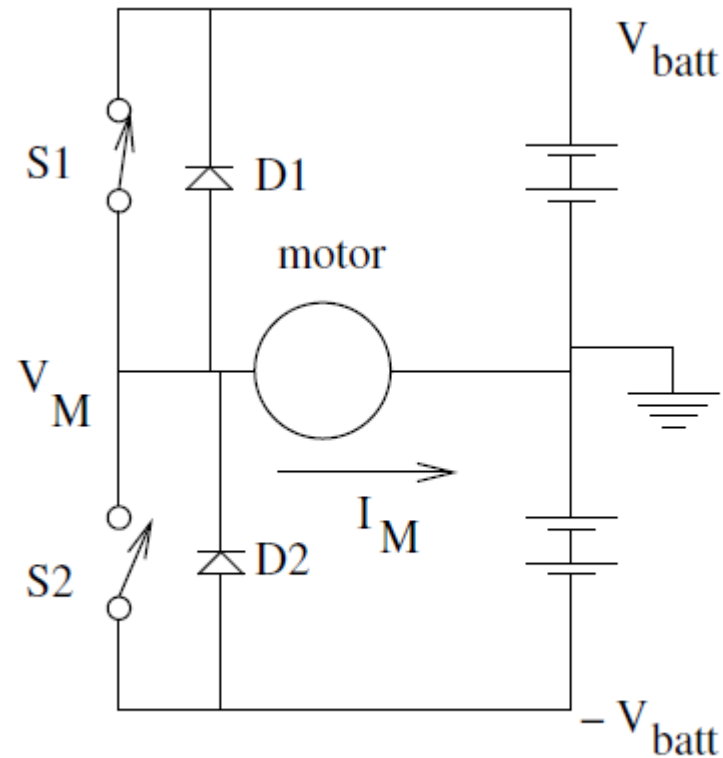

a

# Full-Bridge

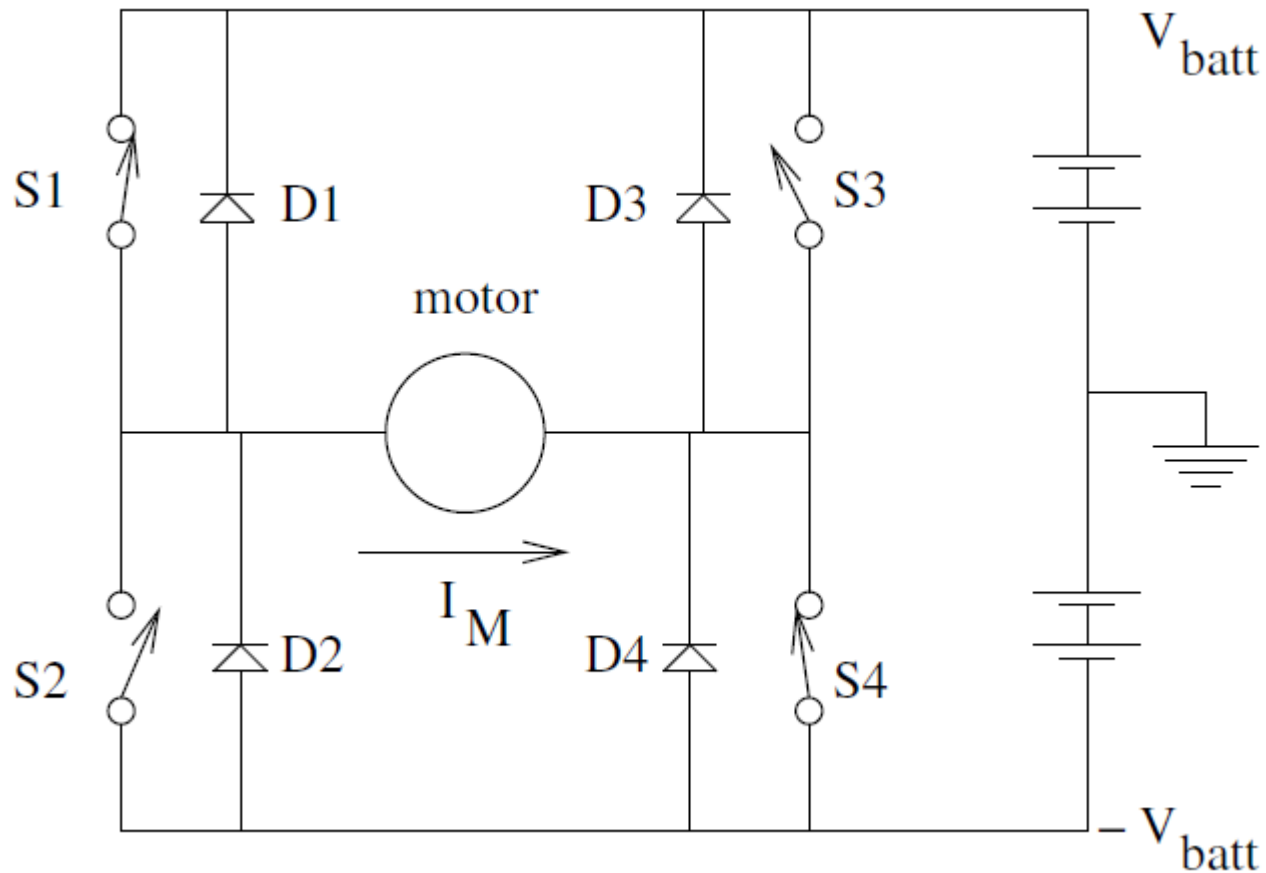

# Motor Brake

---

# A long use of braking...

---



Dynamic Braking resistor from train

Source: <http://www.resistorguide.com/braking-resistor/>



Regenerative Braking on Tesla

Source:


[http://upload.wikimedia.org/wikipedia/commons/5/5c/Tesla\\_Model\\_S\\_P85%2B\\_60\\_kW\\_Regenerative\\_Braking\\_%28cropped%29.jpg](http://upload.wikimedia.org/wikipedia/commons/5/5c/Tesla_Model_S_P85%2B_60_kW_Regenerative_Braking_%28cropped%29.jpg)

# Transistors as Switches

---


# NPN Transistor Operation

---

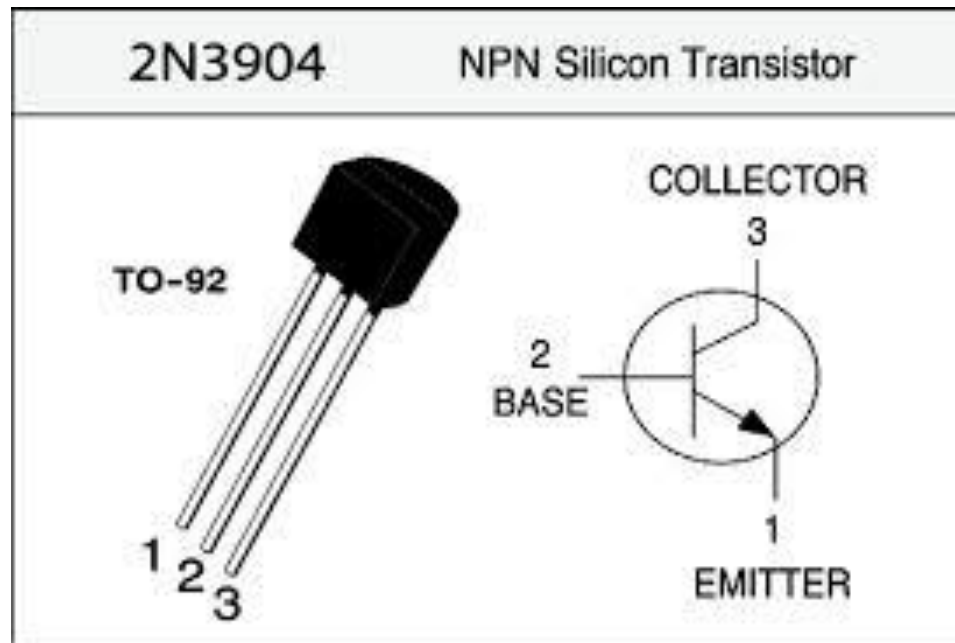


# Current Amplifier

---

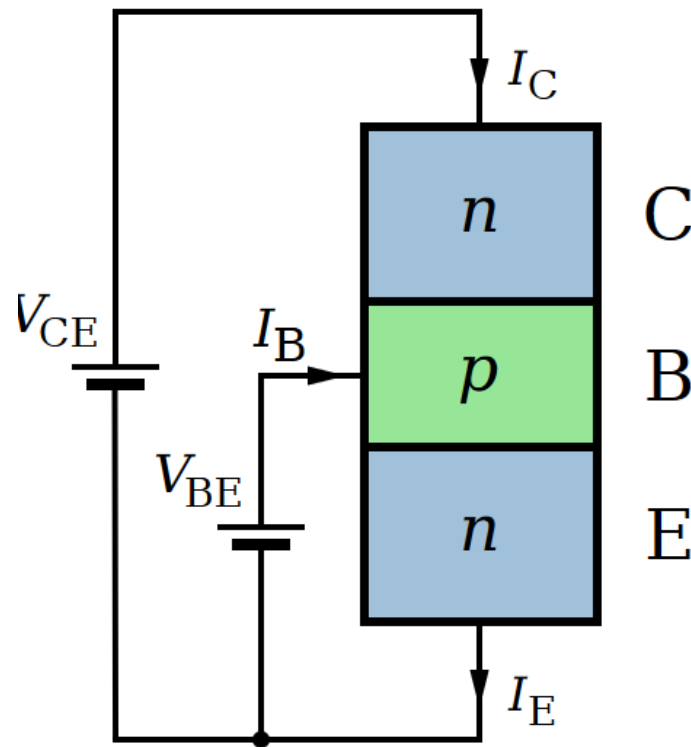

# NPN Transistor Switch


---

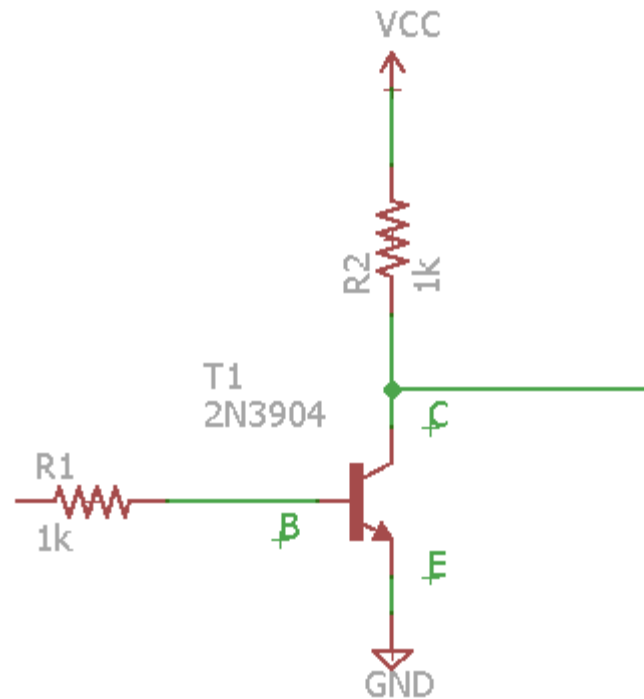




# PNP Transistor Switch

---

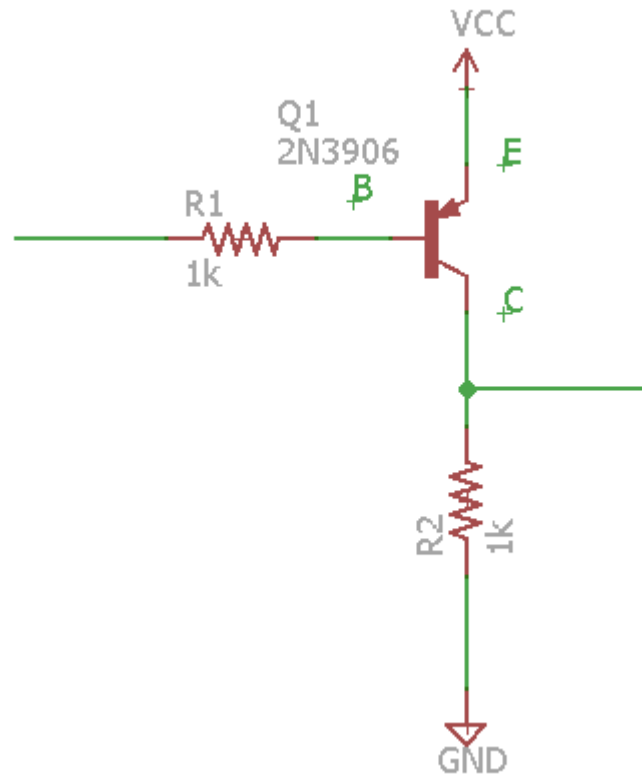

# Example: On/Off Control

---

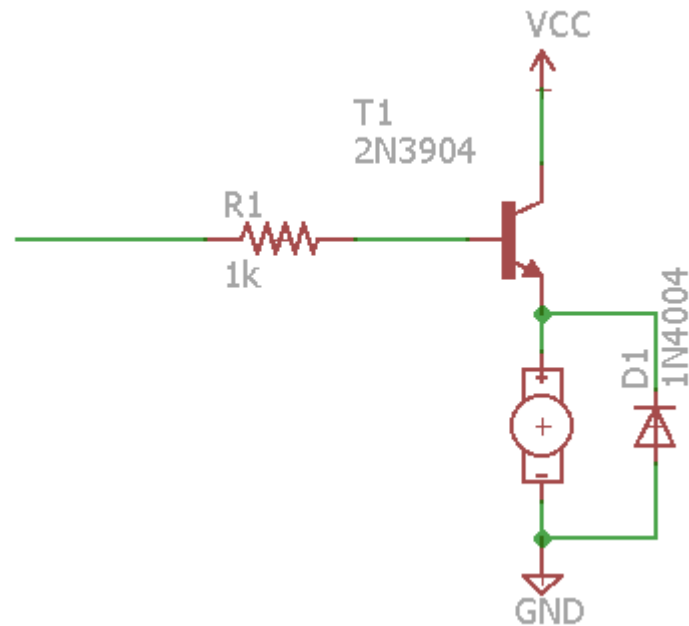

# ...need more power

---

## Absolute Maximum Ratings\*


$T_A = 25^\circ\text{C}$  unless otherwise noted

Symbol	Parameter	Value	Units
$V_{CEO}$	Collector-Emitter Voltage	40	V
$V_{CBO}$	Collector-Base Voltage	60	V
$V_{EBO}$	Emitter-Base Voltage	6.0	V
$I_C$	Collector Current - Continuous	200	mA
$T_J, T_{stg}$	Operating and Storage Junction Temperature Range	-55 to +150	$^\circ\text{C}$

\*These ratings are limiting values above which the serviceability of any semiconductor device may be impaired.

# MOSFETs

---

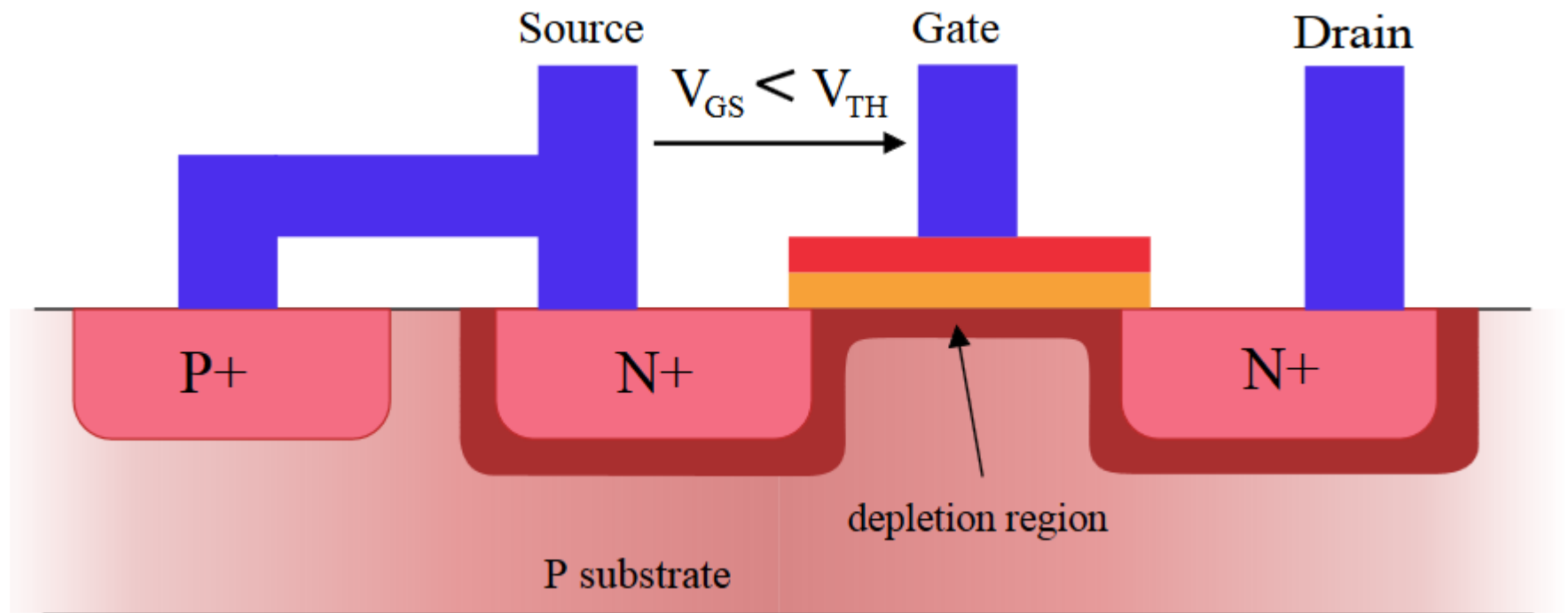

# Quick Comparison



---

Characteristic	MOSFET	Bipolar
Drive Voltage	Medium (1.8V-10V)	Low (< 1V)
Gate current	Low	Medium
Gate charge	Medium	Low
Static Sensitive	Yes	No
Gain vs Temp	Negative	Positive


# MOSFET Types

---

P-Channel

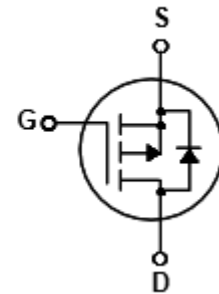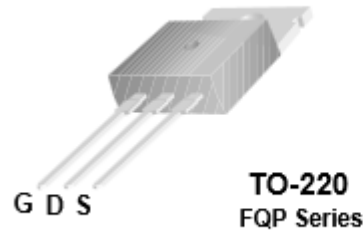


N-Channel

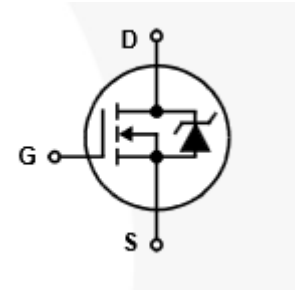


# P-Channel as Switch

---

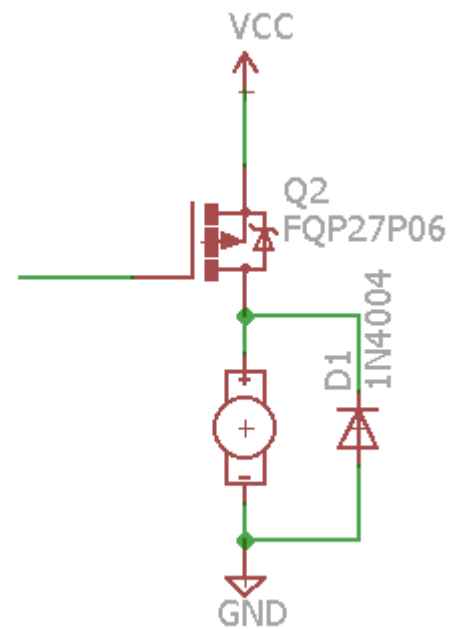

# N-Channel as Switch

---

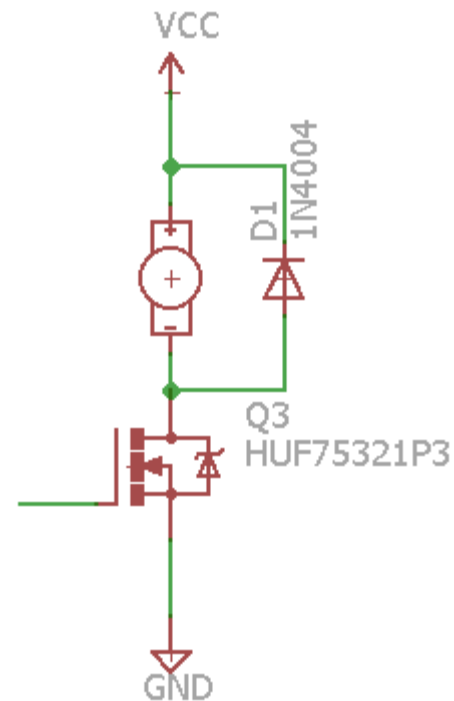



# Note on Gate Capacitance

---

# MOSFET Characteristics

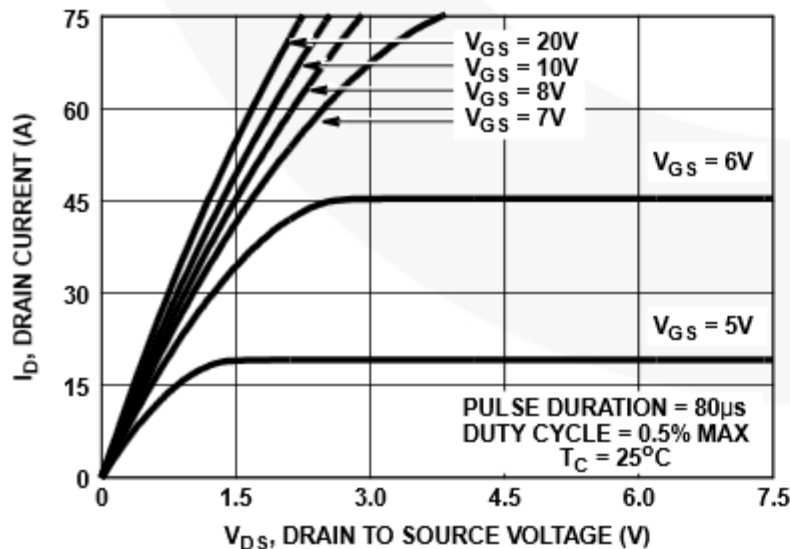


FIGURE 7. SATURATION CHARACTERISTICS


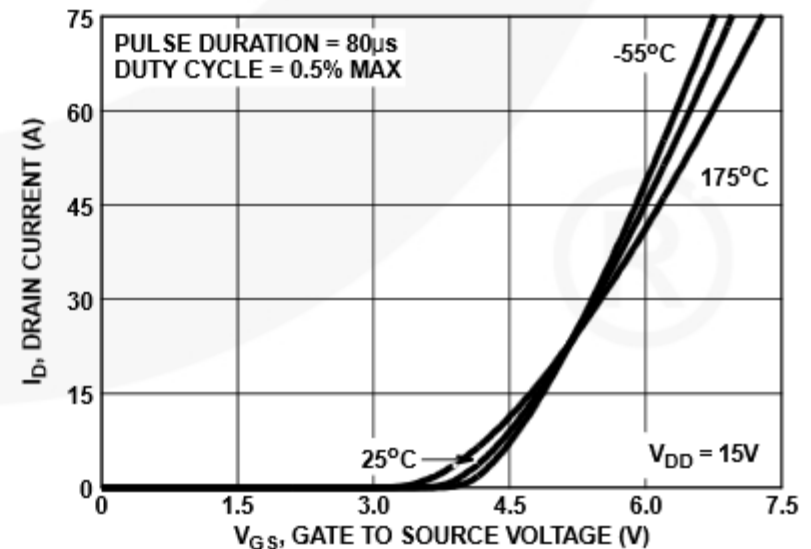



FIGURE 8. TRANSFER CHARACTERISTICS

# Example Half-Bridge Driver

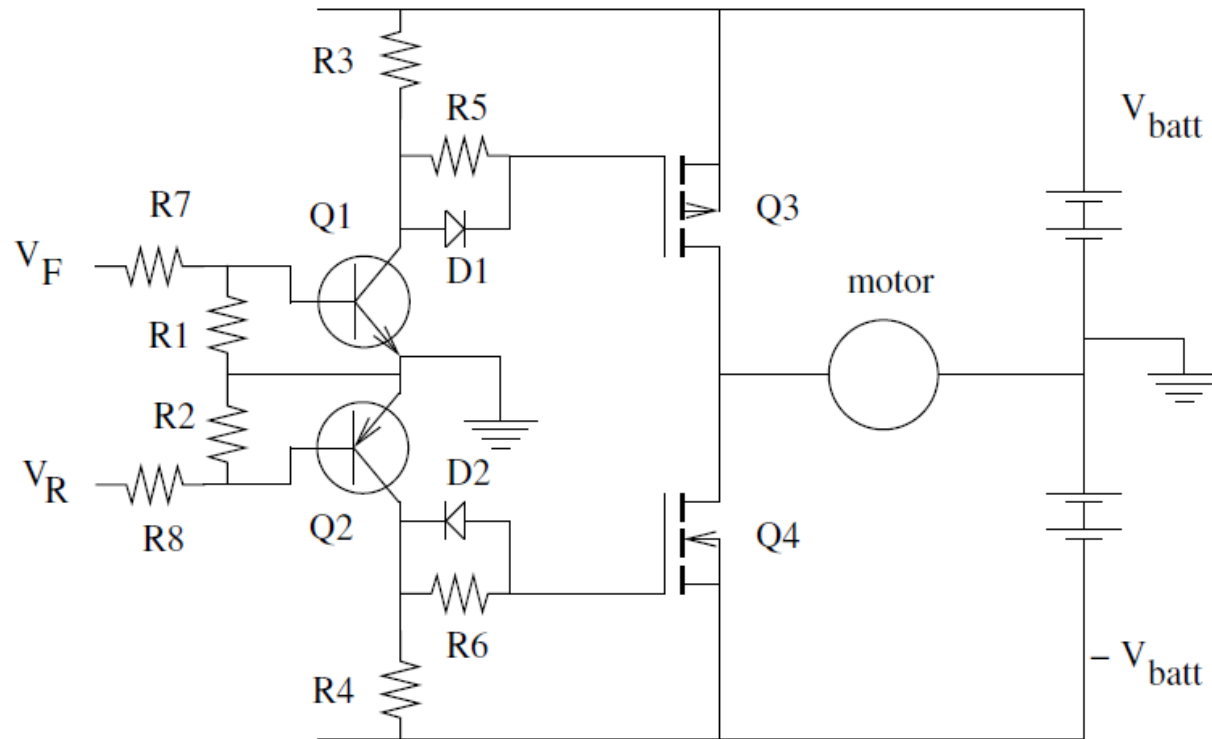


# Slew Rate Tests

---

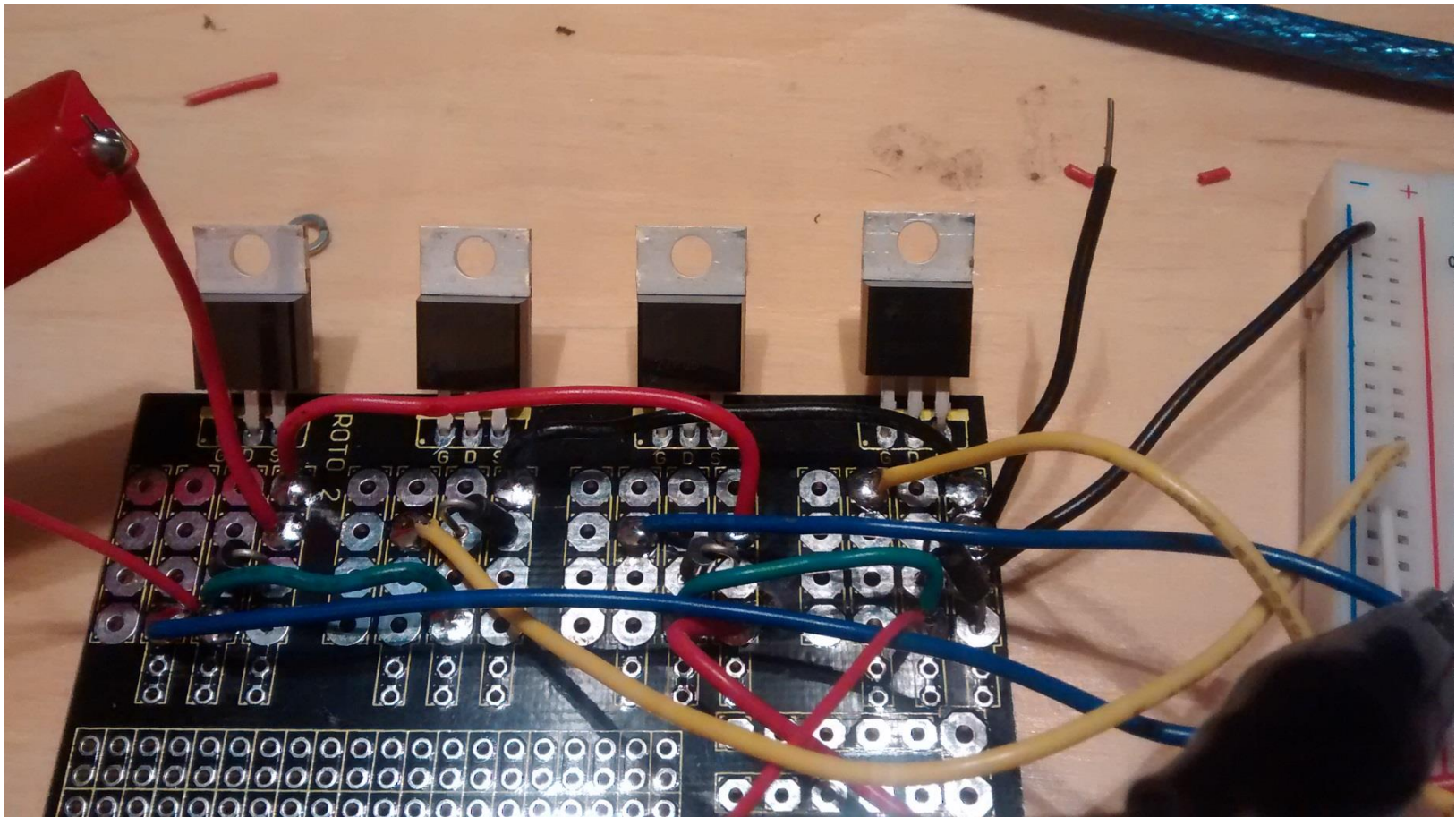


# MOSFET Switching Speed

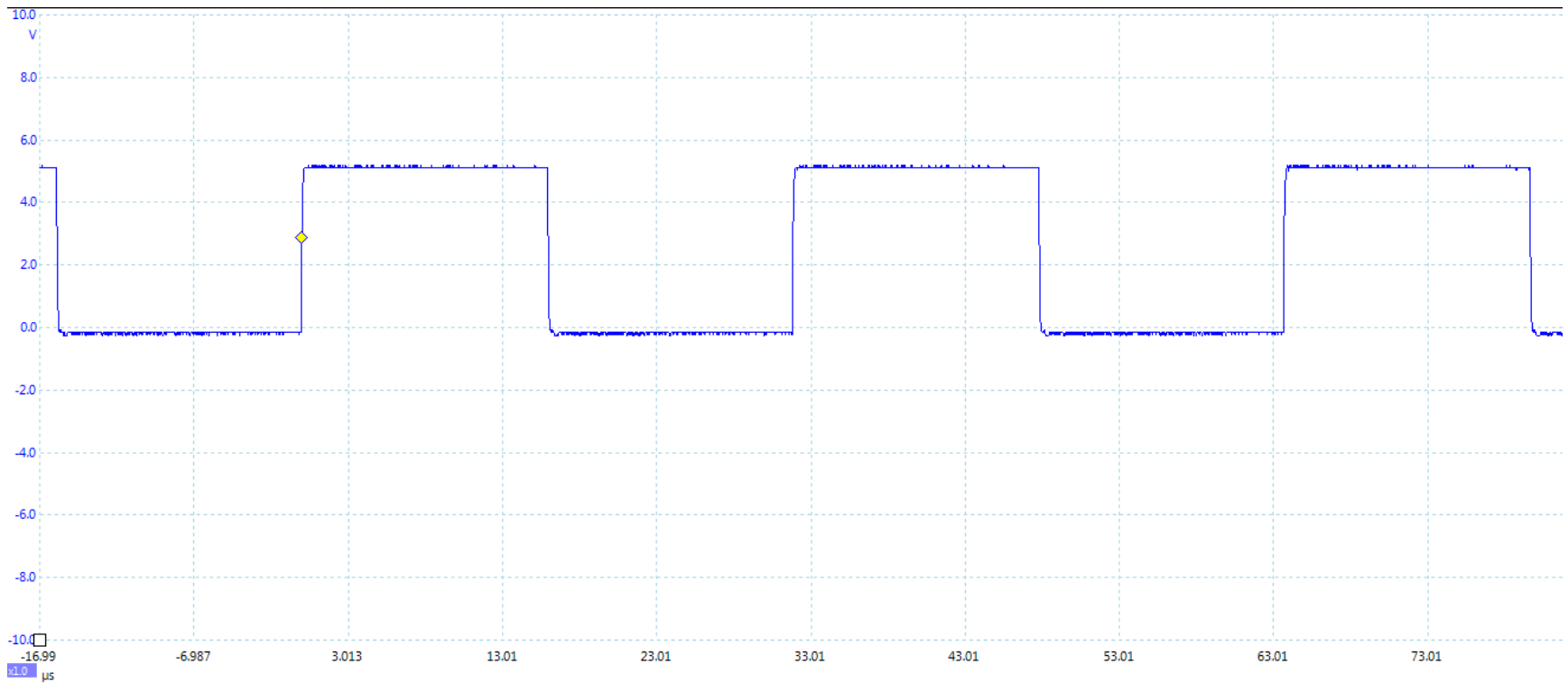


# Fast Slew Rate

---

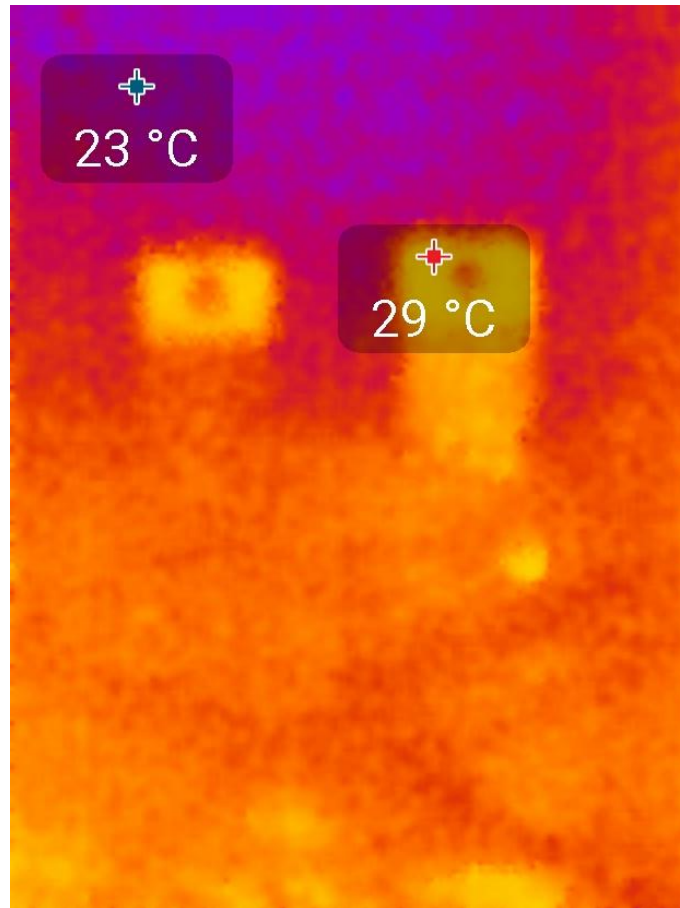


# MOSFET Switching Speed

---

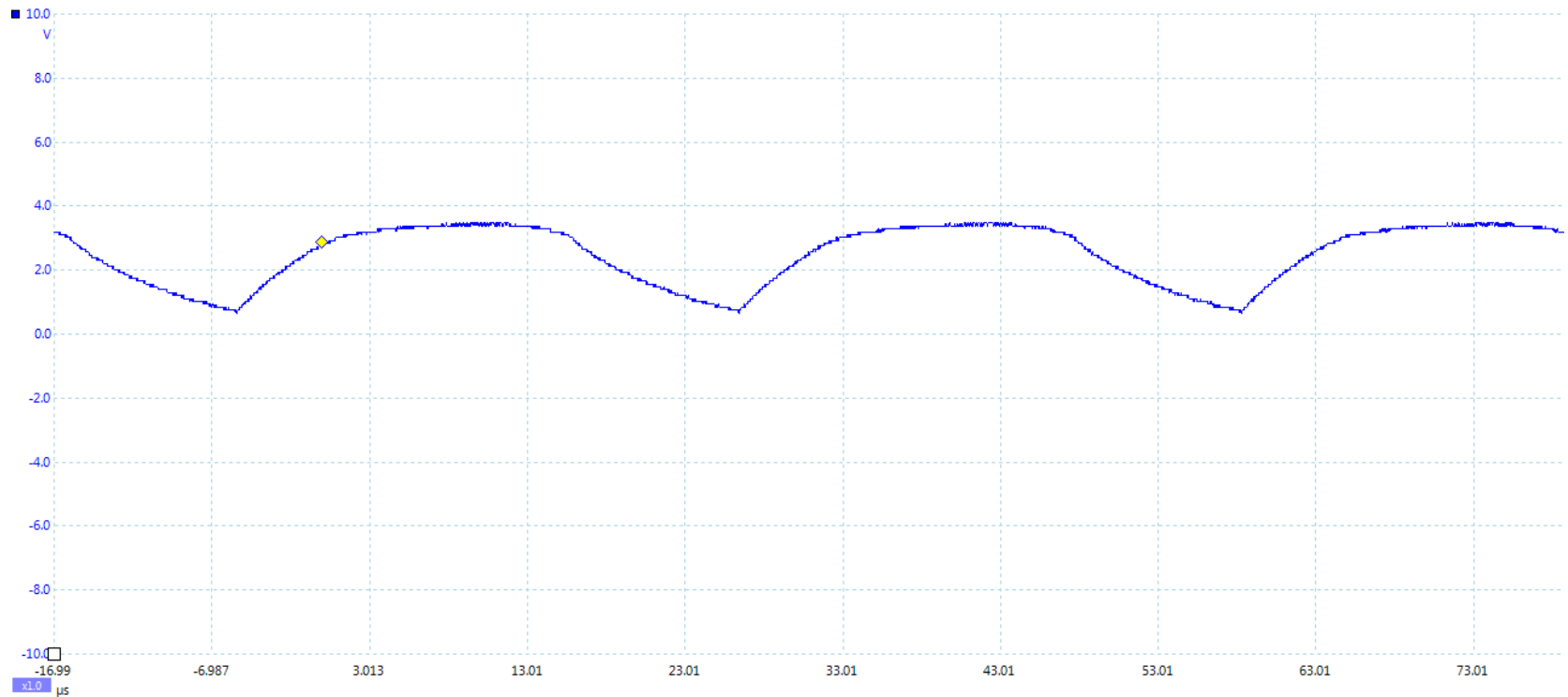

# Slow Slew Rate


---

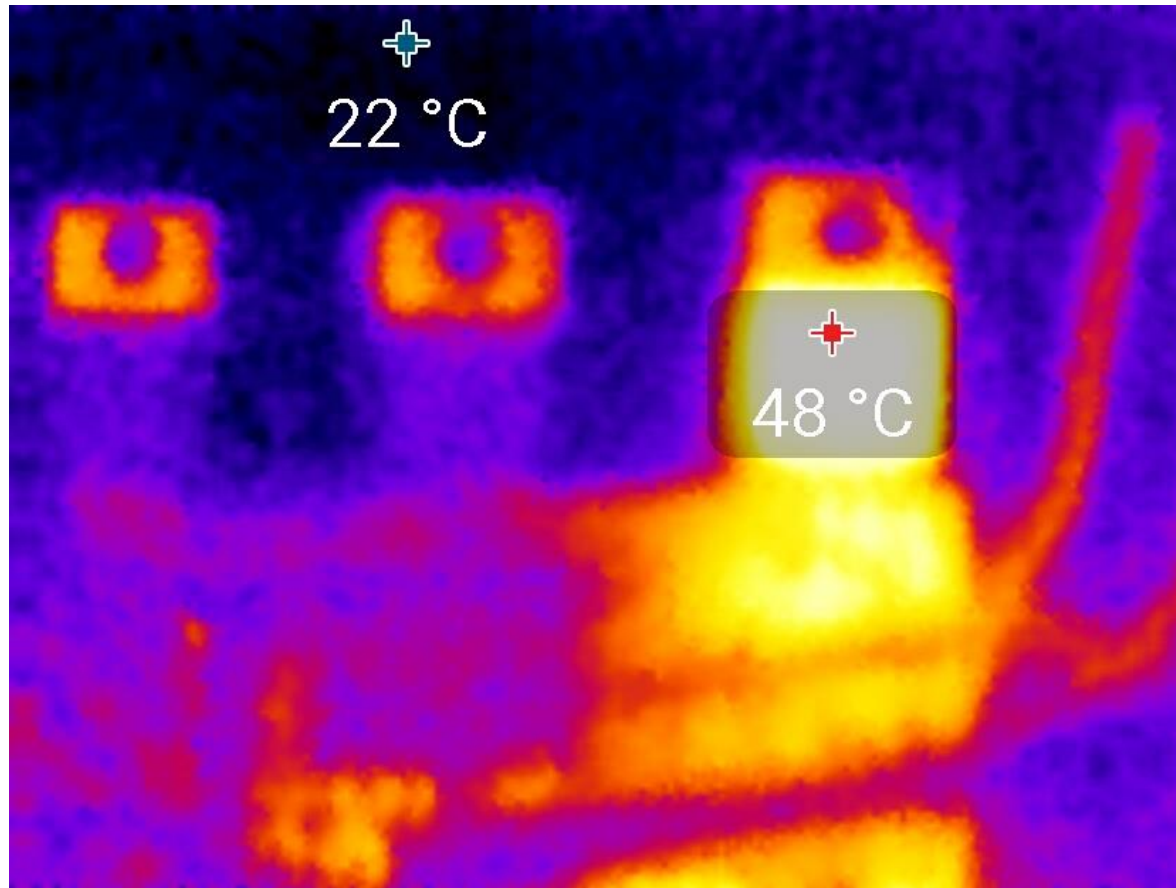




# H-Bridge – Basics (for Lab)

---

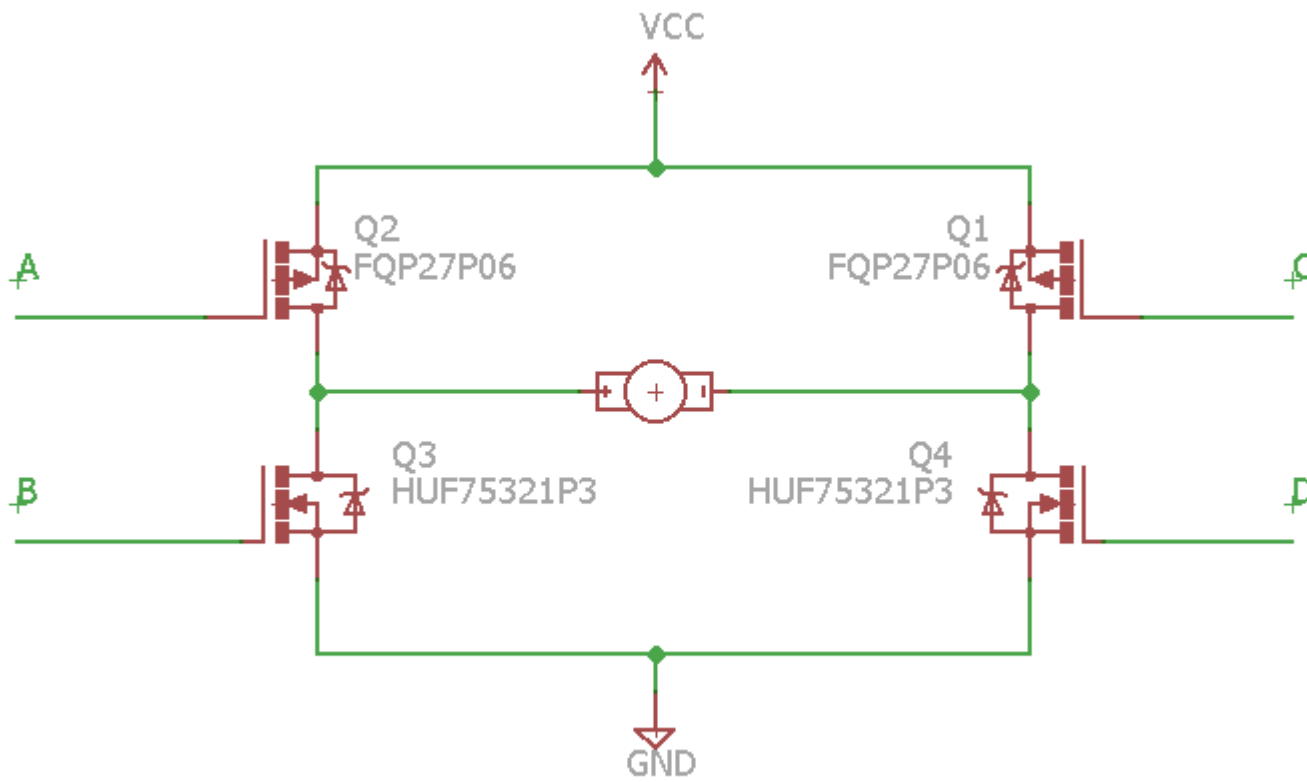

# Avoid smoke...

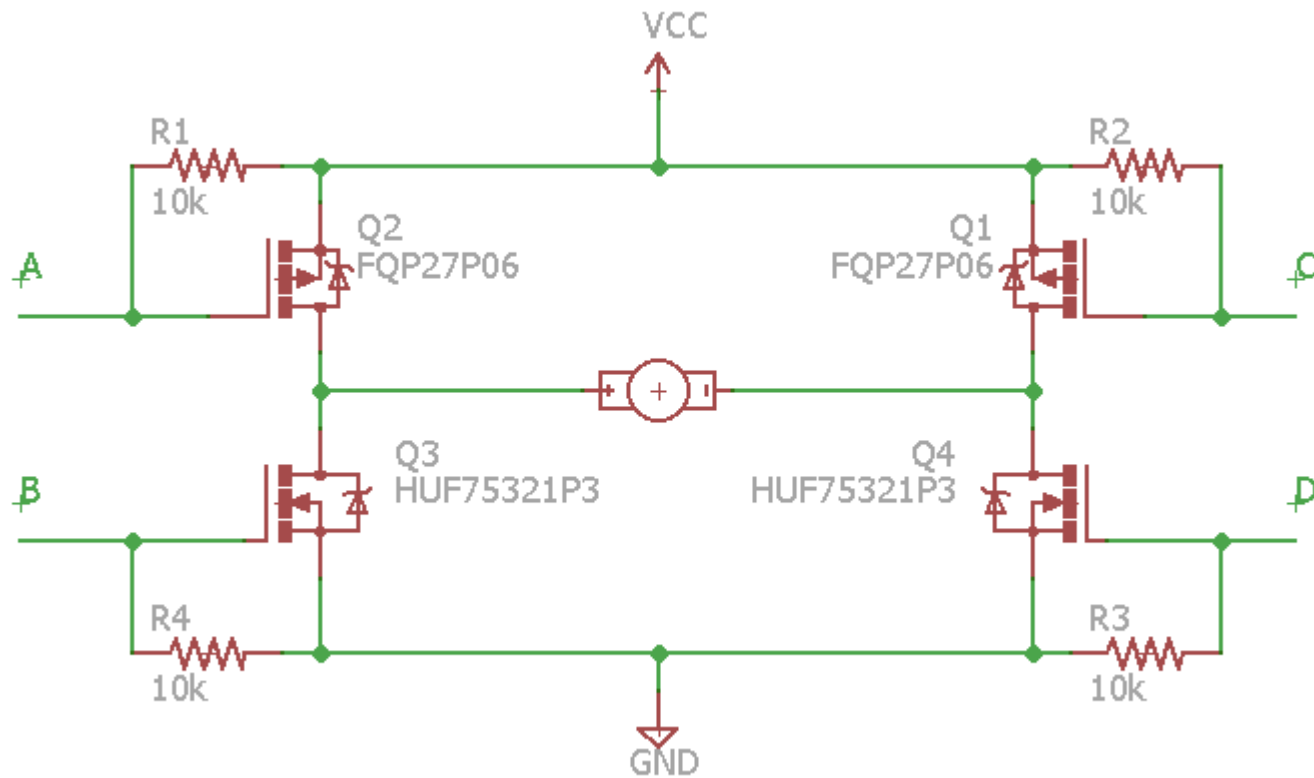

# Your Robot



## 5-A H-Bridge for DC-Motor Applications



### 1 Overview

#### 1.1 Features

- Delivers up to 5 A continuous 6 A peak current
- Optimized for DC motor management applications
- Operates at supply voltages up to 40 V
- Very low  $R_{DS\ ON}$ ; typ. 200 m $\Omega$  @ 25 °C per switch
- Output full short circuit protected
- Overtemperature protection with hysteresis and diagnosis
- Short circuit and open load diagnosis with open drain error flag
- Undervoltage lockout
- CMOS/TTL compatible inputs with hysteresis
- No crossover current
- Internal freewheeling diodes
- Wide temperature range;  $-40\text{ }^{\circ}\text{C} < T_J < 150\text{ }^{\circ}\text{C}$
- Green Product (RoHS compliant)
- AEC Qualified

Type	Package
TLE 5205-2	PG-TO220-7-11

## TLE 5205-2



PG-TO220-7-11




PG-DSO-20-37



PG-TO263-7-1

# Your Robot

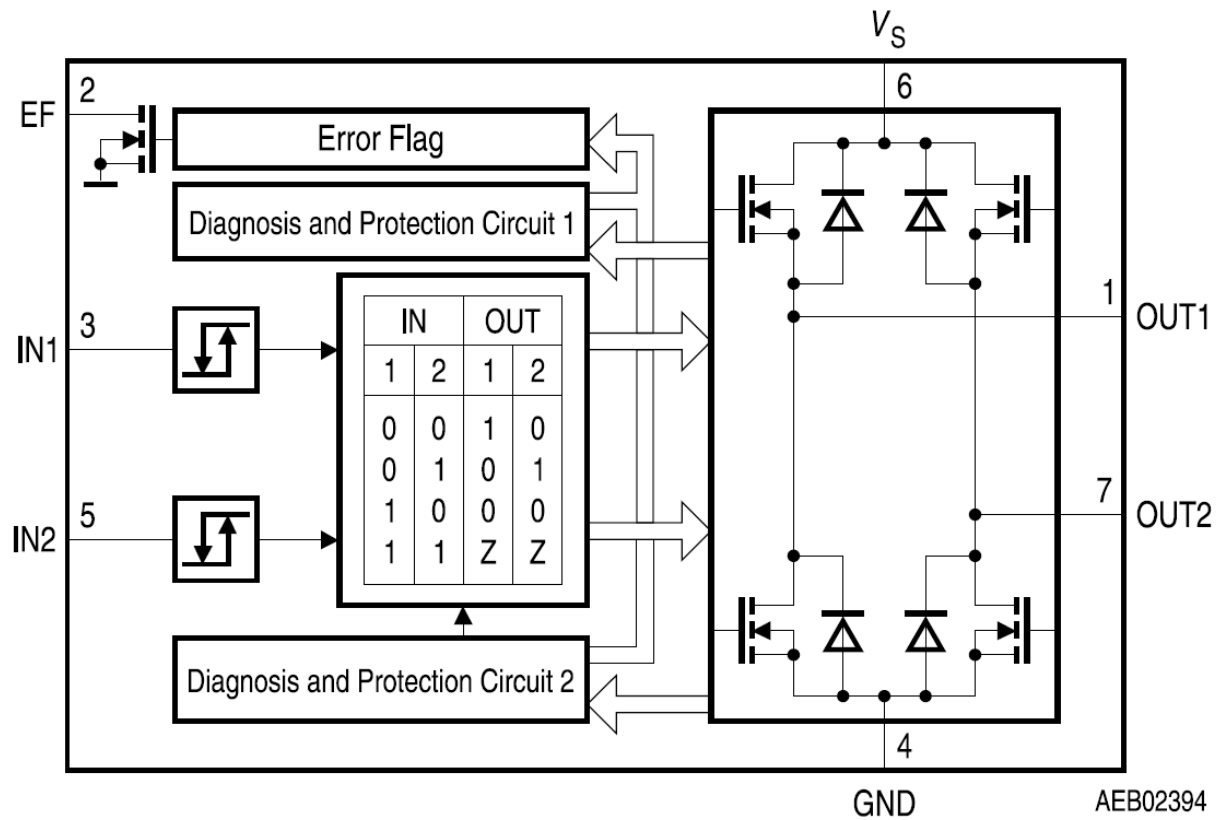

# Summary

---

- Brushed and Brushless DC Motors
- Motors characteristics give us some grief (turn-off spike, noise)
- Use transistors as switch for driving
- Careful design of both MOSFET and Bipolar circuits required